
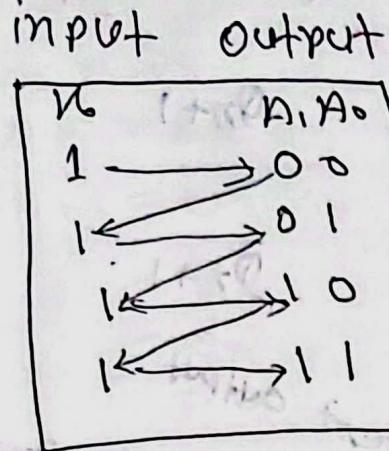


sequential circuit

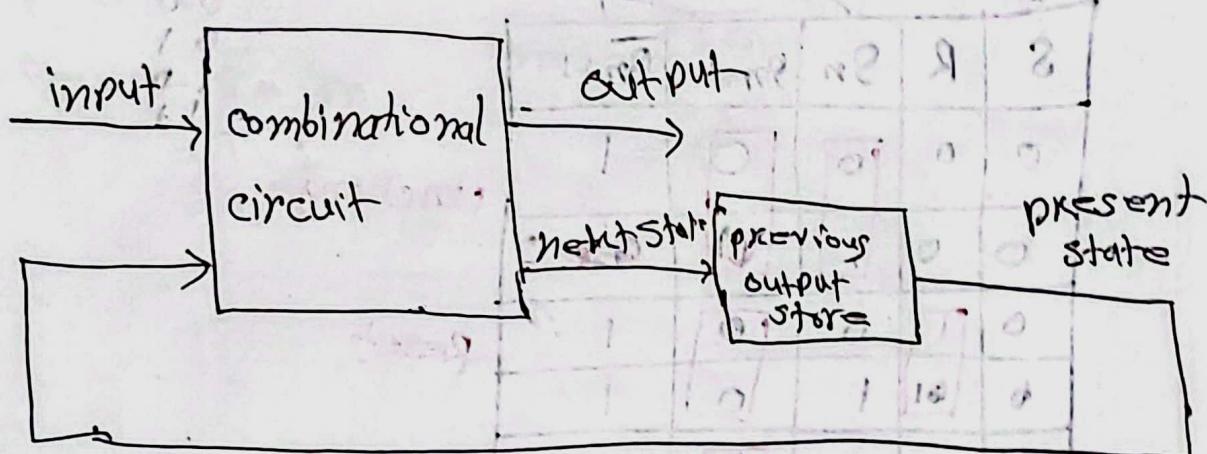

प्रतिक्रिया त्रिज्ये काढ़ा previous
output परी; कर्मान् input द्वारा देखा

Counter circuit




Circuit 2 वर्क्टर

Synchronous sequential circuit → Depend on time


Asynchronous sequential circuit → not depend on time

■ 1 bit store / Latch

■ SR Latch (NOR)

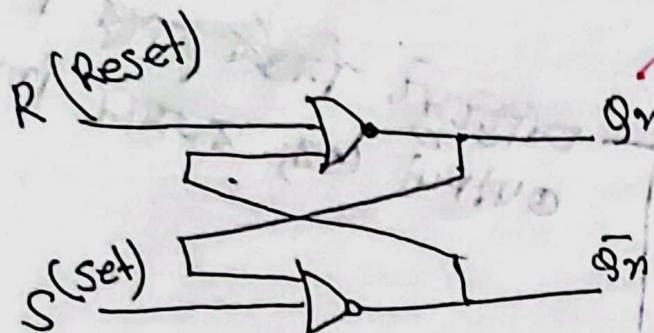

previous output
main output

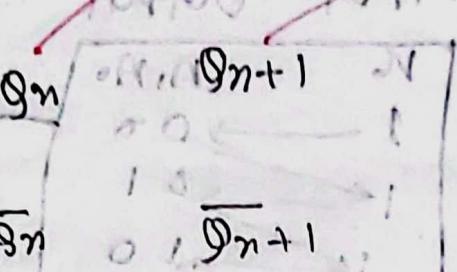

S	R	Q_n	Q_{n+1}	\bar{Q}_{n+1}
0	0	0	0	1
0	0	1	0	0
0	1	0	0	1
0	01	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0		
1	1	1		

priority
previous output
present output

S R
0 0
0 1
1 0
1 1

unchange
Reset

set

} undefined

$S, R = 0$ आणि Q_n सर आणि Q_{n+1} 1

Set, Reset एवं ट्राई SR Latch लोग ट्राई आणि
1 आणि 0 आणि compare घेवा नाही फिरू झाले।

Q_{n+1} හෝ \bar{Q}_{n+1} යෙහි පැහැදු රාජ්‍ය පොදු දූග්‍රම

න්‍යුත්!

$$\begin{aligned} S=0, R=0 \\ Q_{n+1} &= \overline{R + \bar{Q}_n} \\ Q_{n+1} &= \overline{0 + \bar{Q}_n} \\ &= \overline{\bar{Q}_n} \\ &= \bar{Q}_n \\ &= 0 \end{aligned}$$

$$\begin{array}{c} S=0 \quad R=0 \\ \hline Q_{n+1} = \overline{S+\bar{Q}_n} \\ = \overline{0+\bar{Q}_n} \\ = \overline{\bar{Q}_n} \\ = 1 \end{array}$$

S	R	Q_{n+1}	\bar{Q}_{n+1}
0	0	0	1
0	1	0	1
1	0	1	0
1	1	1	1


$$S=0 \quad R=1$$

$$\begin{aligned} Q_{n+1} &= \overline{R + \bar{Q}_n} \\ &= \overline{1 + 1} \\ &= 0 \end{aligned}$$

$$\begin{aligned} Q_{n+1} &= \overline{S+\bar{Q}_n} \\ &= \overline{0+0} \\ &= 1 \end{aligned}$$

↓ Invalid

input	output
SR	$Q_{n+1} \quad \bar{Q}_{n+1}$
00	unchange
01	0 1
10	1 0
11	undefined

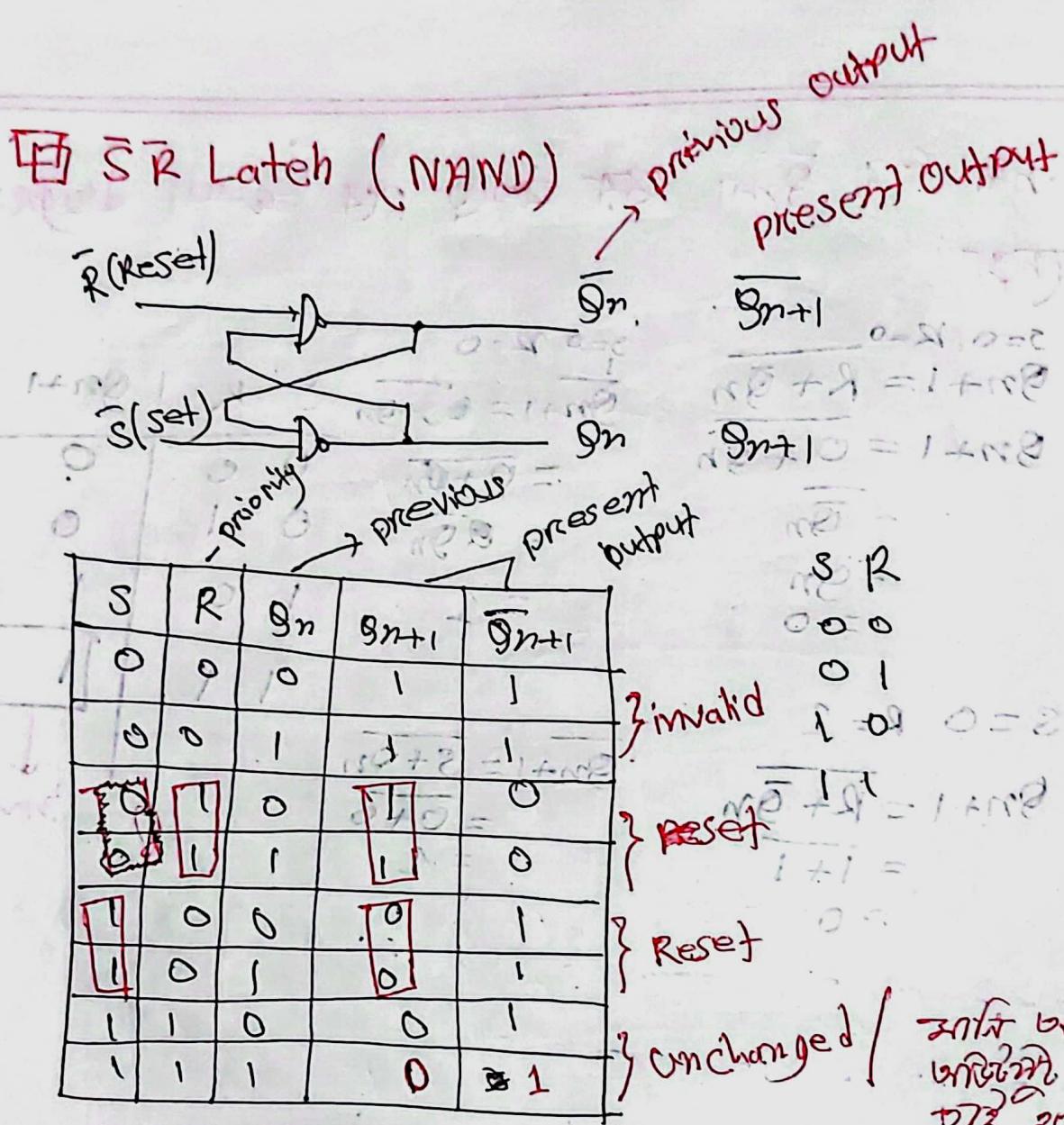

প্রথম SR NOR এর চিহ্ন

$S=0, R=0$, invalid পদ্ধতি \bar{Q}_{n+1} ০; \bar{Q}_{n+1} ১
 মাত্র বিনাশ পদ্ধতি কথা কিংবা কাস্টম পদ্ধতি

S_{n+1} (Q_2); \bar{Q}_{n+1} get from diagram

$$S=0, R=0$$

$$\begin{aligned} Q_{n+1} &= \overline{S + \bar{Q}_n} \\ &= \overline{0 + \bar{Q}_n} \\ &= 1 \end{aligned}$$

$$S=0, R=1$$

$$\begin{aligned} Q_{n+1} &= \overline{S \cdot \bar{Q}_n} \\ &= \overline{0 \cdot \bar{Q}_n} \\ &= 1 \end{aligned}$$

S, R	Q_{n+1}	\bar{Q}_{n+1}
0 0		
0 1	1	0
1 0	0	1
1 1		

S	R	Q_{n+1}	\bar{Q}_{n+1}
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	1

$$Q_{n+1} = \overline{R \cdot Q_n}$$

$$= 1$$

S	R	Q_{n+1}	\bar{Q}_{n+1}
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	1

Q_{n+1}

invalid

1 0

0 1

unchange

$S \neq R$ | Q_{n+1} \bar{Q}_{n+1}

0 1 | 1 0

0 1 | 1 0

1 0 | 0 1


1 1 | 0 1

0 0 | 1 1

possible

NT

SR Latch with control / flip-flop

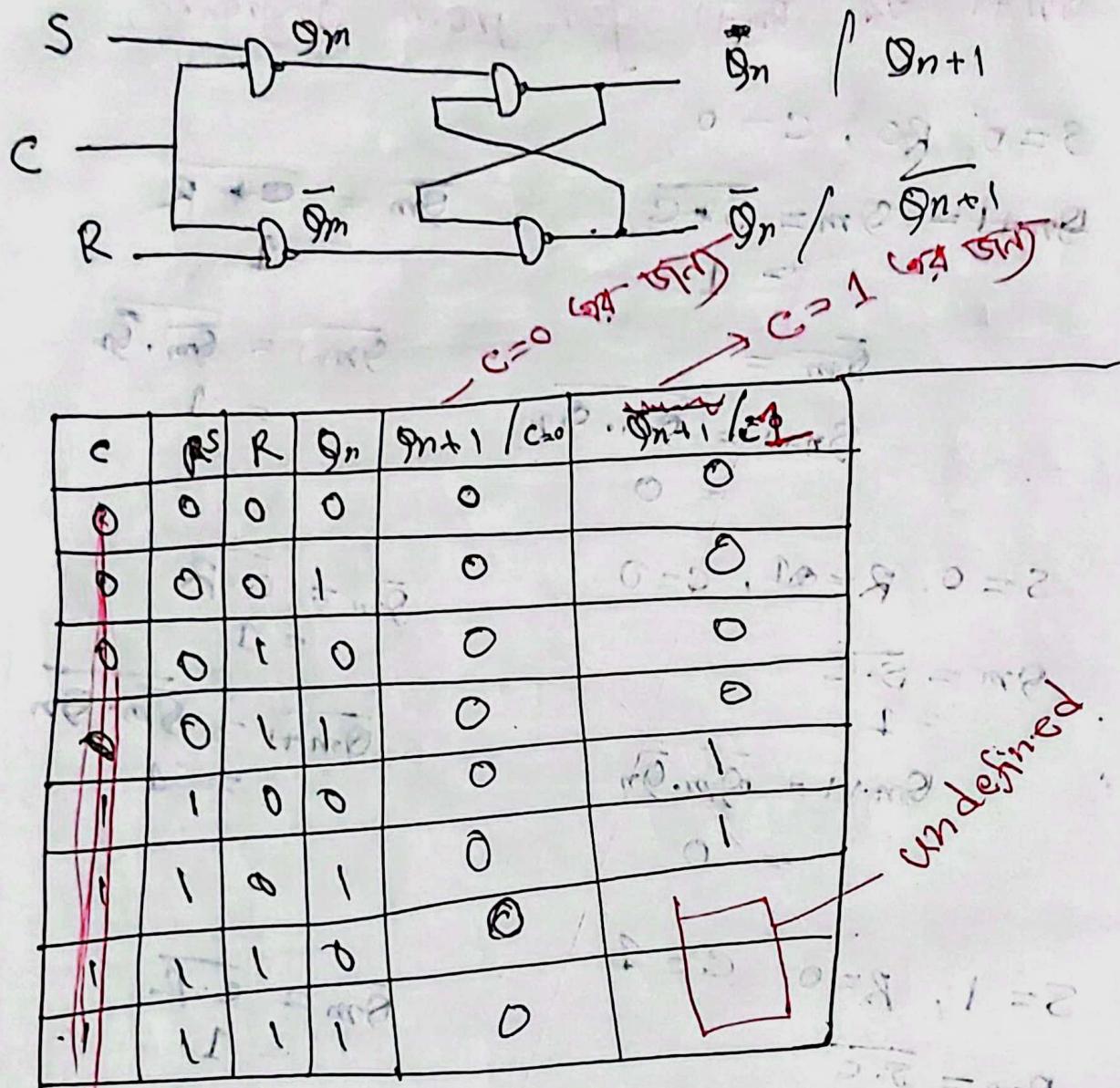

प्रश्नात् यदि विद्युतीय SR Latch का- 2T2R
प्राप्ति दर्शाति- उत्तम Q_m का; \bar{Q}_m का (2) SR का
2T2R प्राप्ति दर्शाति 2T2R का।

$$\textcircled{X} \quad C=0, S=0, R=0, \bar{Q}_n = 0$$

$$Q_m = 1$$

$$Q_n = \frac{\bar{Q}_m \cdot \bar{Q}_n}{1 \cdot 1} \\ = 0$$

$$\bar{Q}_m = 1$$

$$\bar{Q}_n = \frac{Q_m \cdot Q_n}{0 \cdot 1} \\ = 1$$

clock

$$\textcircled{X} \quad C=0, S=0, R=0, \bar{Q}_n = 0$$

$$Q_m = 1$$

$$Q_n = \frac{Q_m \cdot Q_n}{\bar{Q}_m \cdot \bar{Q}_n} \\ = 0$$

$$\bar{Q}_m = 1$$

$$\bar{Q}_n = \frac{\bar{Q}_m \cdot \bar{Q}_n}{Q_m \cdot Q_n} \\ = 1$$

$$C=1, S=0, R=0, \bar{Q}=0$$

$$Q_m = 1$$

$$\bar{Q}_n = \frac{Q_m \cdot Q_n}{1 \cdot 1} \\ = 0$$

$$\bar{Q}_m = 1$$

$$\bar{Q}_n = \frac{\bar{Q}_m \cdot \bar{Q}_n}{1 \cdot 0} \\ = 1$$

$$\textcircled{X} \quad C=0, S=1, R=0, \bar{Q}=0$$

$$Q_m = 1$$

$$Q_n = \frac{Q_m \cdot Q_n}{\bar{Q}_m \cdot \bar{Q}_n} \\ = 1 \cdot 1 \\ = 0$$

$$\bar{Q}_m = 1$$

$$\bar{Q}_n = \frac{\bar{Q}_m \cdot \bar{Q}_n}{Q_m \cdot Q_n} \\ = 1 \cdot 0 \\ = 1$$

$$C=1, S=0, R=1, \bar{Q}=1$$

$$Q_m = 1$$

$$\bar{Q}_n = \frac{Q_m \cdot Q_n}{1 \cdot 0} \\ = 0$$

$$\bar{Q}_m = 0$$

$$\bar{Q}_n = \frac{\bar{Q}_m \cdot \bar{Q}_n}{0 \cdot 1} \\ = 1$$

$$\textcircled{X} \quad C=0, S=1, R=1, \bar{Q}_n = 1$$

$$Q_m = 1$$

$$\bar{Q}_m = 1$$

$$Q_n = \frac{Q_m \cdot Q_n}{\bar{Q}_m \cdot \bar{Q}_n} \\ = 0$$

$$\bar{Q}_n = \frac{\bar{Q}_m \cdot \bar{Q}_n}{Q_m \cdot Q_n} \\ = 1 \cdot 0 \\ = 1$$

invalid
state change

$$C=1, S=1, R=0, \bar{Q}_n = 0$$

$$Q_m = 0$$

$$\bar{Q}_n = \frac{Q_m \cdot Q_n}{0 \cdot 1} \\ = 1$$

$$\bar{Q}_n = 1$$

$$\bar{Q}_n = \frac{\bar{Q}_m \cdot \bar{Q}_n}{1 \cdot 0} \\ = 0$$

$$C=1, S=1, R=1, \bar{Q}_n \neq 1$$


$$Q_m = 0$$

$$\bar{Q}_n = \frac{Q_m \cdot Q_n}{0 \cdot 0} \\ = 1$$

$$\bar{Q}_n = 0$$

$$\bar{Q}_n = \frac{\bar{Q}_m \cdot \bar{Q}_n}{0 \cdot 1} \\ = 0$$

D Latch / Flip-Flop

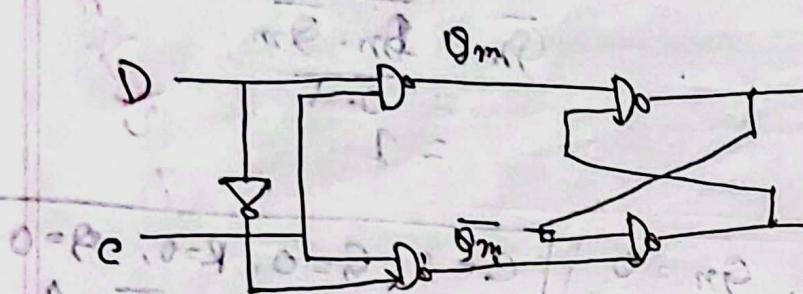

\varnothing	\varnothing_n	\varnothing_m	\varnothing_m	\varnothing_n .	\varnothing_{n+1}	\varnothing_{n+1}
0	0	1	1	..	0	1
0	1	1	1	0	0	1
1	0	1	0		1	0
1	1	0	1		1	0

$C = O - D$

$C \rightarrow$ O_n O_n
 $D \rightarrow$ unchanged

$$\begin{array}{r} \cancel{0} = \cancel{m} \\ \cancel{m} \cdot \cancel{m} = \cancel{m} \\ \cancel{1} \cdot \cancel{1} = \cancel{1} \\ \cancel{1} = \cancel{1} \end{array}$$

0 0 0 0 0
0 0 0 0 0
0 0 0 0 0
0 0 0 0 0

$$Q_n = 0$$

$$C = 0 \quad D = 0$$

$$Q_m = \overline{D \cdot C} \\ = \overline{0 \cdot 0} \\ = 1$$

$$Q_{n+1} = \overline{Q_m \cdot \bar{Q}_n} \\ = \overline{1 \cdot 1} \\ = 0$$

$$C = 0, \quad D = 1 \quad Q = 0$$

$$Q_m = 1$$

$$\overline{Q_m} = \frac{1}{1+0^2}$$

$$Q_{n+1} = \overline{Q_m \cdot \bar{Q}_n} \\ = \overline{1 \cdot 1} \\ = 0$$

$$\overline{Q_{n+1}} = \overline{\overline{Q_m} \cdot \bar{Q}_n} \\ = \overline{\frac{1}{1+0^2} \cdot 0} \\ = \overline{\frac{1}{1}} \\ = 1$$

$$C = 1 \quad D = 0, \quad Q = 0$$

$$Q_m = 1$$

$$\overline{Q_m} = 0$$

$$Q_{n+1} = 0$$

$$C = 1 \quad D = 1, \quad Q = 0$$

$$Q_m = 0$$


$$\overline{Q_m} = -0 \quad 1$$

$$Q_{n+1} = 1$$

$$\overline{Q_{n+1}} = 0$$

$$\left. \begin{array}{l} Q_n = 1 \\ \overline{Q_{n+1}} = 0 \end{array} \right\} \text{Zur Zeit } t$$

T Latch

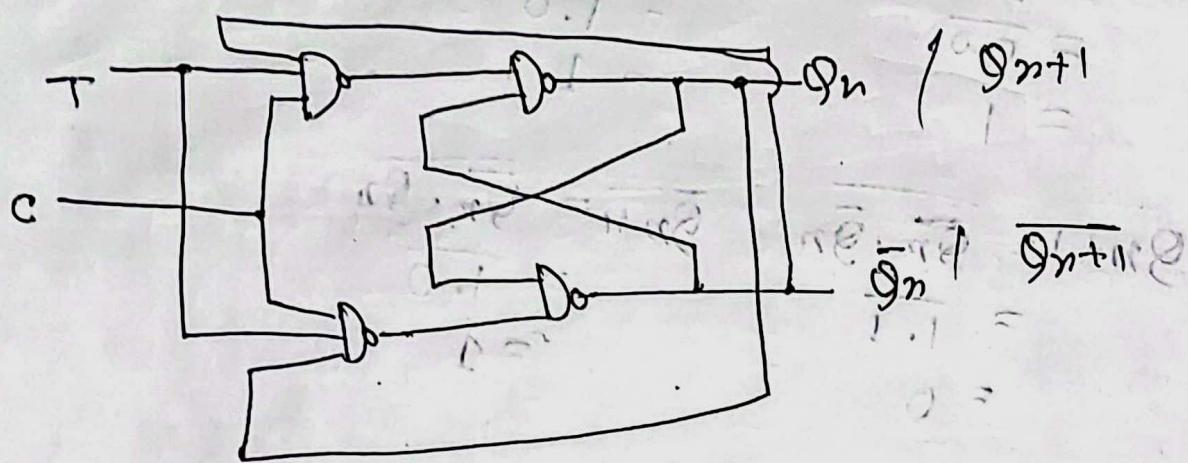

T	Q_n	Q_{n+1}
0	0	$\overline{Q_n} = \overline{0} = 1$
0	1	$\overline{Q_n} = \overline{1} = 0$
1	0	$\overline{Q_n} = \overline{0} = 1$
1	1	$\overline{Q_n} = \overline{1} = 0$




$T=0$ Q_n 2nd bit set

$T=1$ 2nd Q_n Toggle

T Q_n Q_{n+1}
0 X unchange



$T=0$ {
 1
 0 $Q_n = \overline{0} = 1$
 0 $Q_n = \overline{1} = 0$

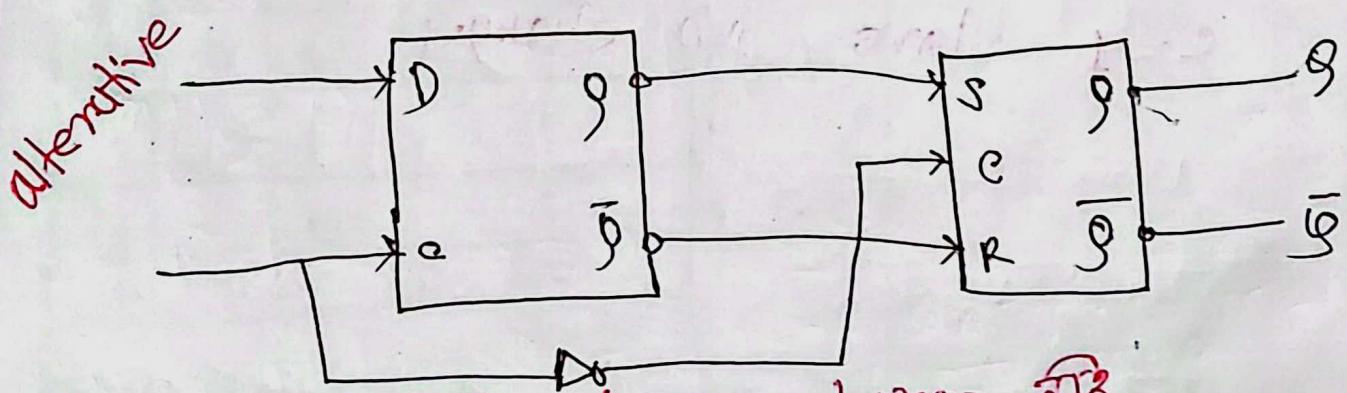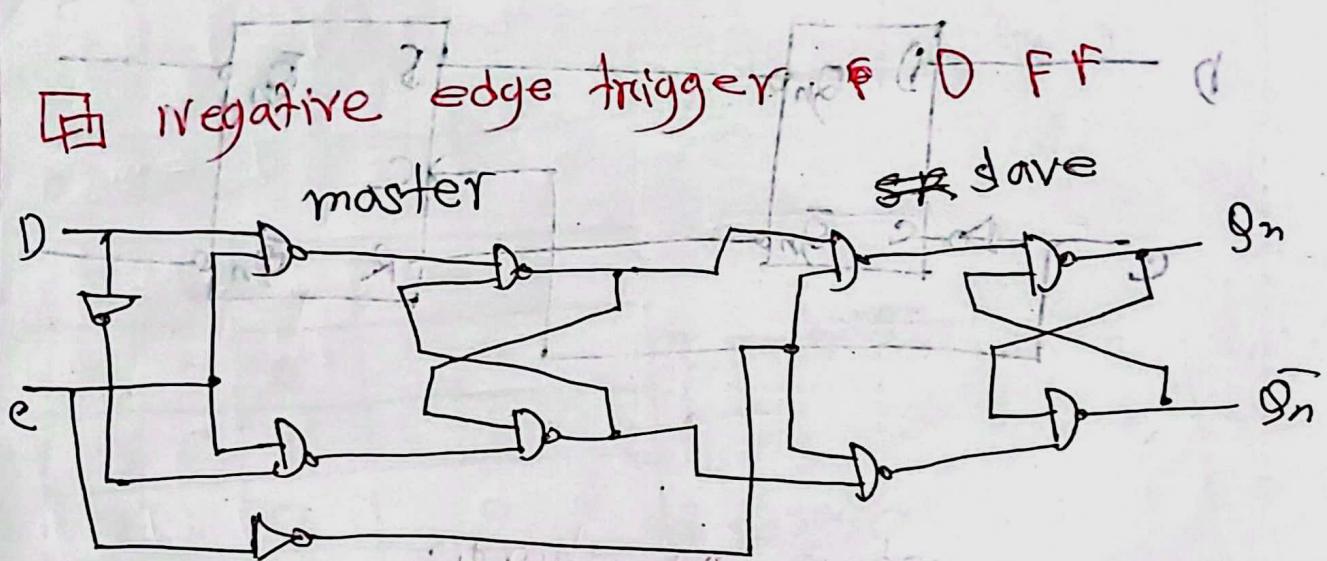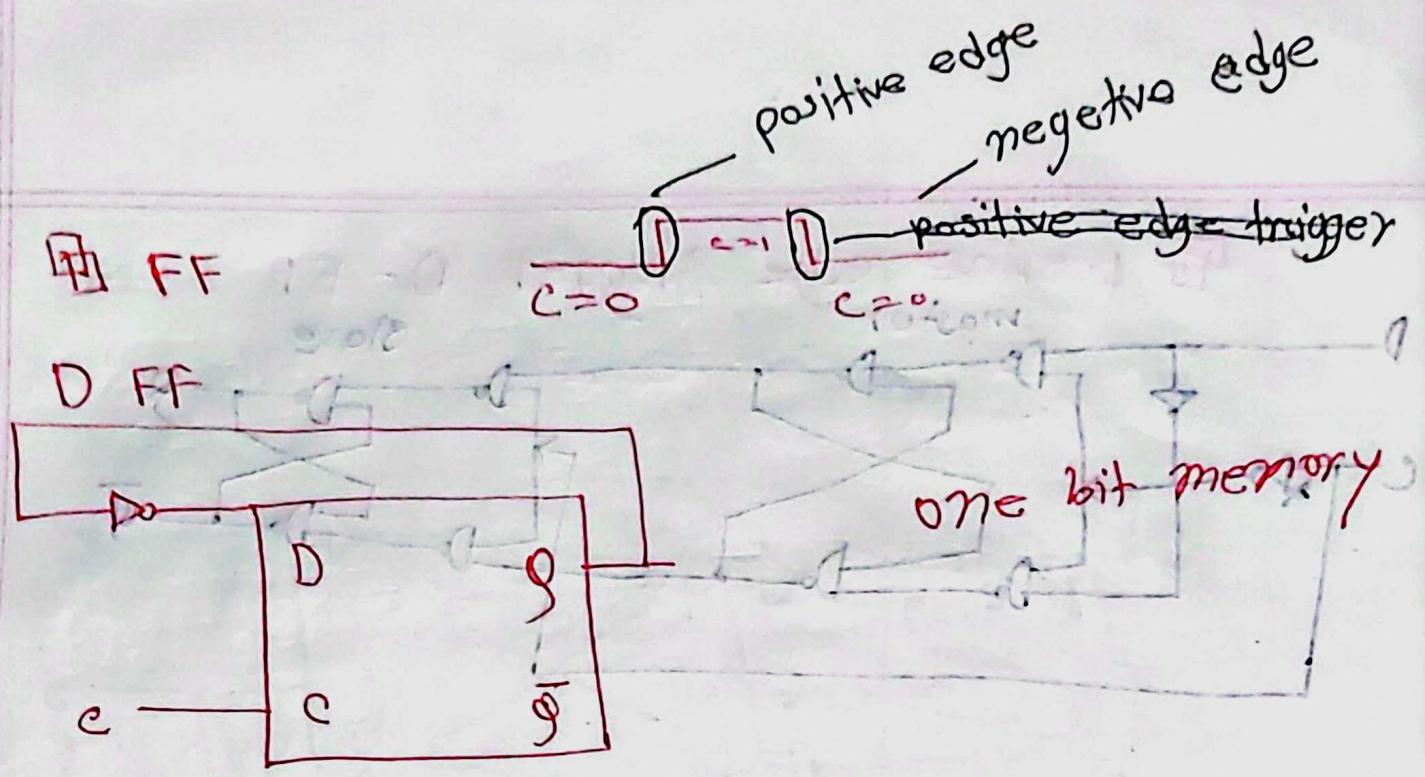$Q_n = \overline{0} = 1$ $T = 1 \rightarrow 0$



$c=0$ થાએલે master ને રોક્ખ કરું change નથી
 $c=1$ થાએલે slave ને રોક્ખ કરું change નથી

positive edge trigger D-FF

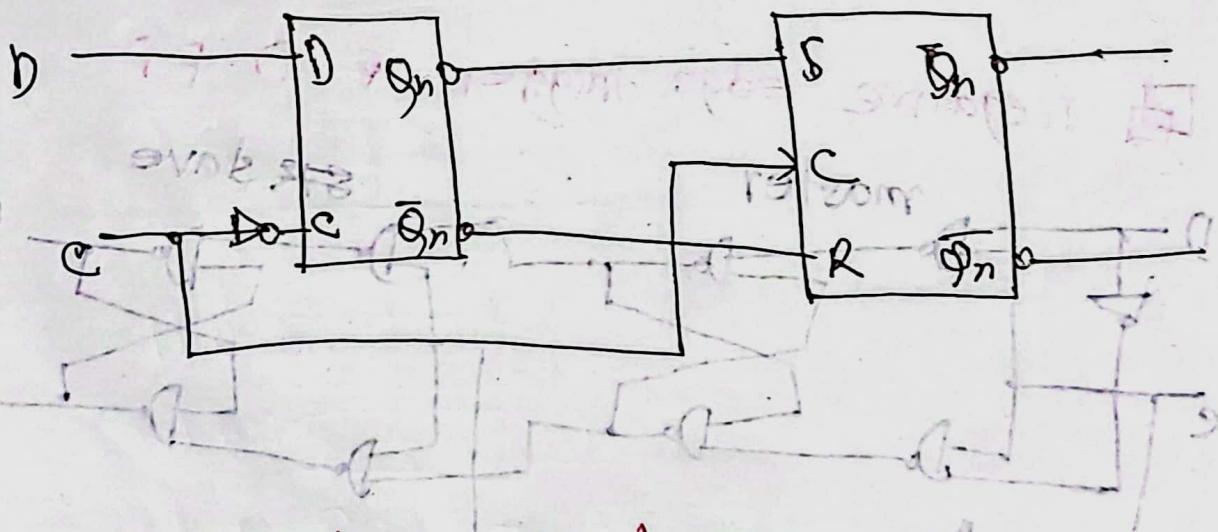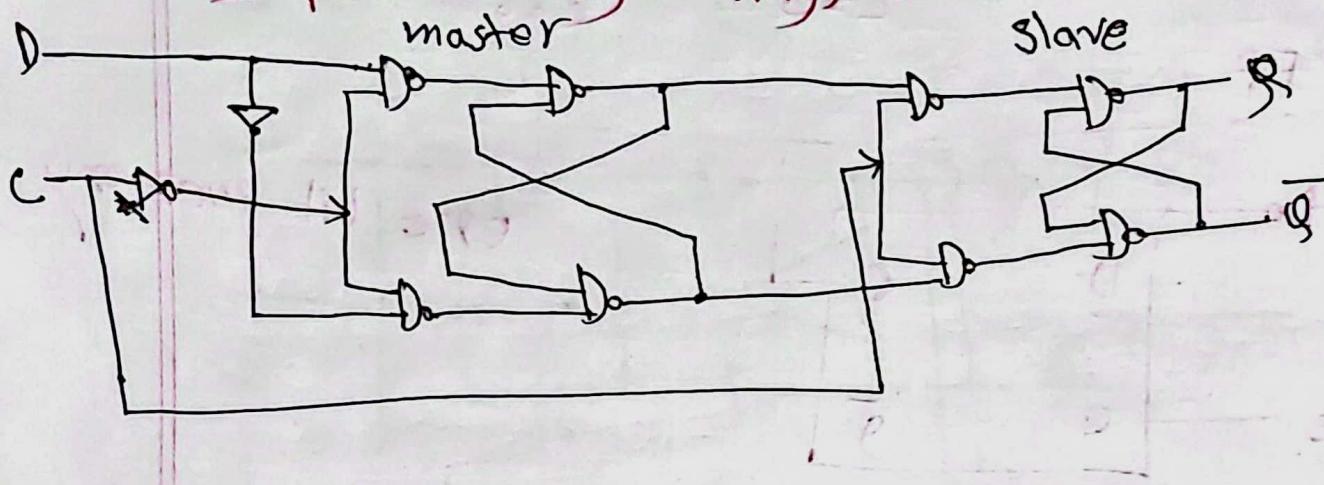


$C = 0$ master no change

$C = 1$ slave no change

JK flip-flop

~~positive edge trigger D FF~~

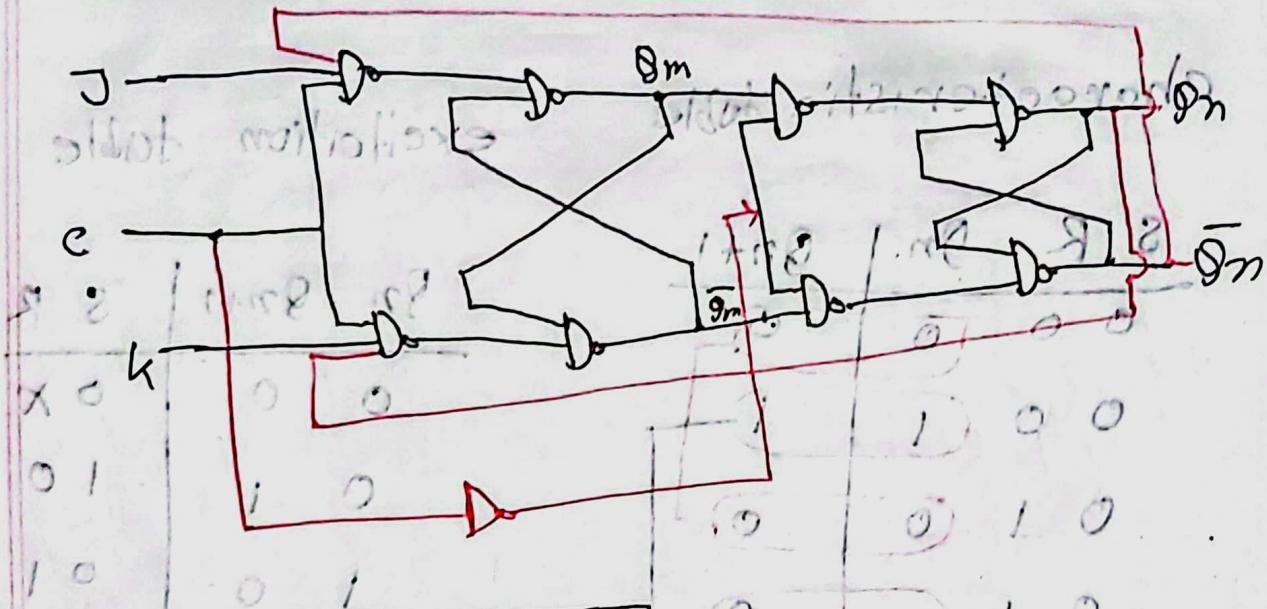

J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	1	0	1
1	1	1	0

no change

reset

set

toggle

means 21 VTC GTR SCRT

Excitation table (ব্যবহার ক্ষেত্র)

SR Latch এর excitation table (XOR)

Characteristic table		excitation table			
S	R	Q_n	Q_{n+1}	S	R
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	0	1	0
		invalid			

Excitation table এবং Characteristic table দেখা ক্ষেত্র

অসম্ভব Q_n এবং Q_{n+1} এর মান দুটি ক্ষেত্রে ১।

যেটা ক্ষেত্র আছে তিনি করবে। উক্ত ক্ষেত্রে don't care ক্ষেত্র এই।

D FF GR excitation table

Characteristic table

D	Q_n	Q_{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

Excitation table

	Q_n	Q_{n+1}	D
0	0	0	0
0	1	1	1
1	0	0	0
1	1	0	1

T FF GR excitation table

Characteristic table

T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

Excitation table

	Q_n	Q_{n+1}	T
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

All most & XOR Com-3 NOR

JK SR Excitation table

Characteristic table

Excitation table

J	K	S _n	S _{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
		0	0

S _n	S _{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	1	0

T	Q _n	Q _{n+1}
0	0	0
1	1	0
1	0	1
0	1	1

Q _n	Q _{n+1}	T
0	0	0
0	1	0
1	0	1
1	1	1

આન્ડ એન્ડ શરૂઆત - ટાબ �excitation table
 ડાયાલ શરૂઆત ટાબ �characteristic table

■ FF conversion

D To T to FF conversion,

T	Q _n	Q _{n+1}	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

Q _n	Q _{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1


T to D FF conversion

D	Q _n	Q _{n+1}	T
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

Q _n	Q _{n+1}	T
0	0	0
0	1	1
1	0	0
1	1	1


D	Q _n	Q _{n+1}
0	0	1
1	1	0
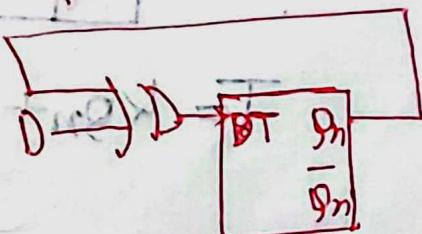
$$\begin{aligned} T &= \bar{D}Q_n + D\bar{Q}_n \\ &= D \oplus Q_n \end{aligned}$$



T to JK FF conversion


J k, Q _n	Q _{n+1}	T	Q _n Q _{n+1}	J	K
0 0	0 0	0	0 0	0	0
0 0	1 0	0	0 1	1	0
0 1	0 0	0	1 1	0	0
1 0	1 1	1	1 1	0	1
1 0	0 1	1	0 1	1	1
1 0	1 1	0	1 0	1	1
1 1	0 0	1	1 1	1	1

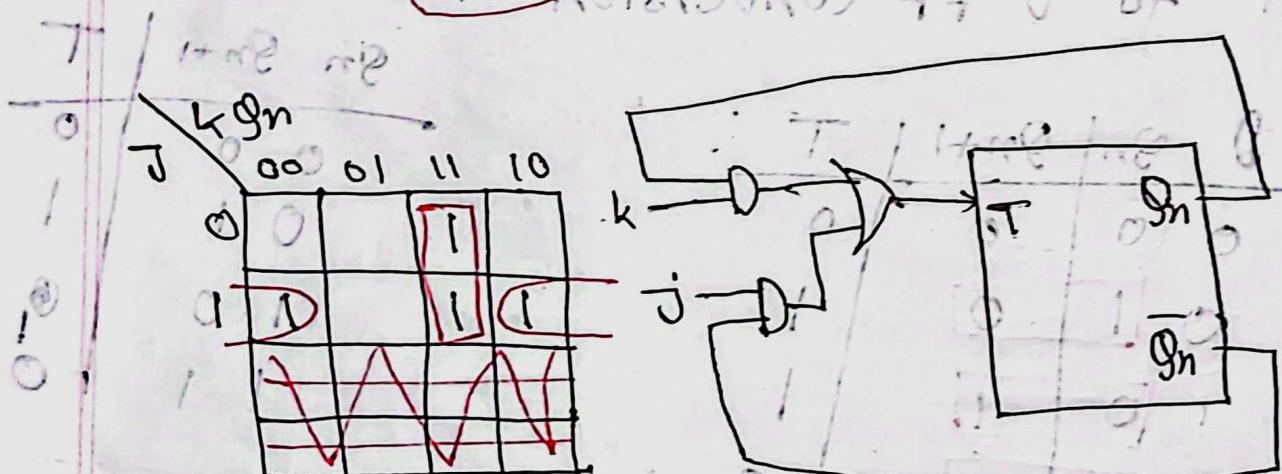

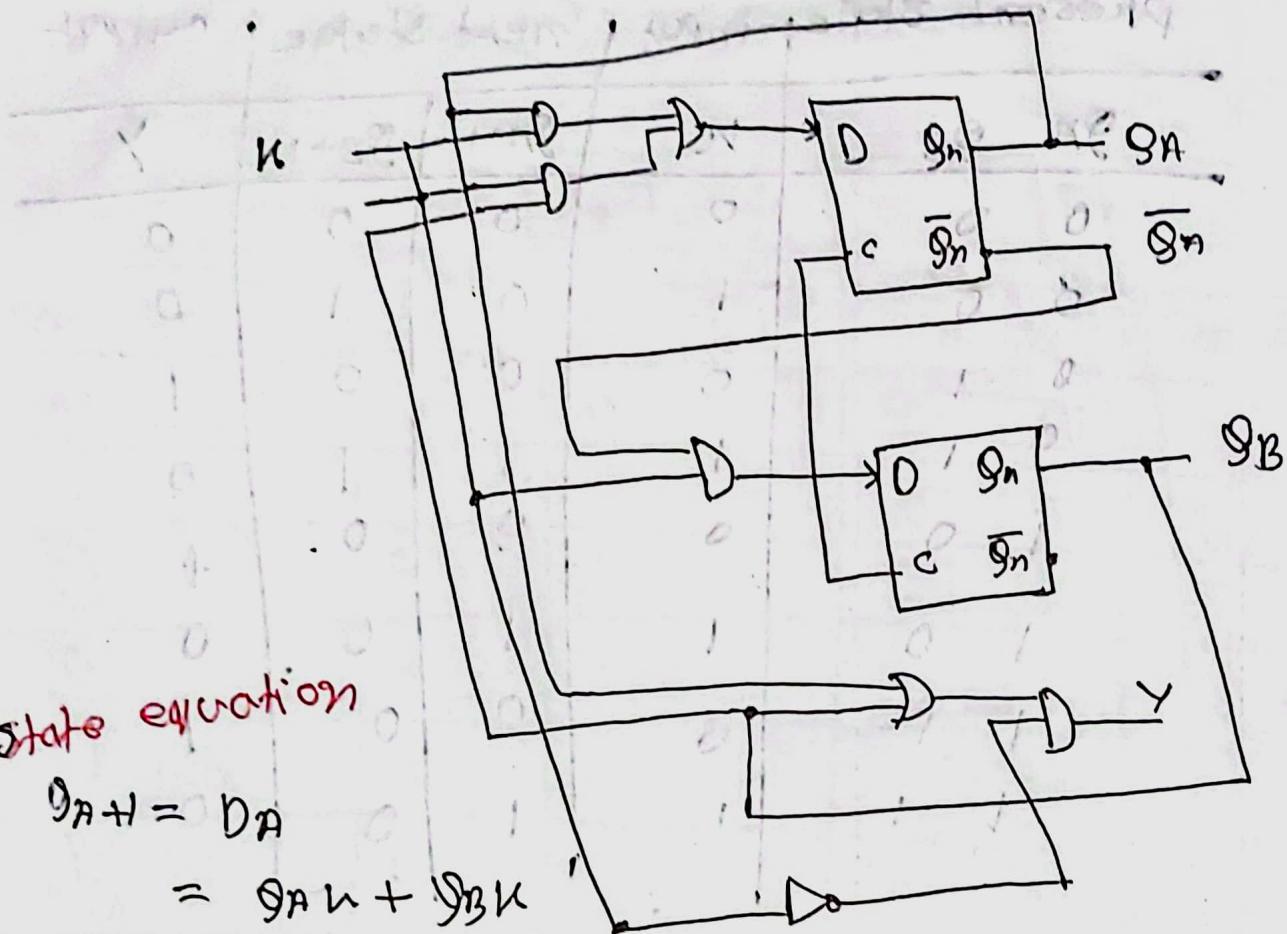problem

slide 43.

Analysis of sequential circuit : state / transition equation




① State equation

$$\begin{aligned}Q_{A+1} &= D_A \\&= Q_A n + Q_B K\end{aligned}$$

$$\begin{aligned}Q_{B+1} &= D_B \\&= \bar{Q}_n n\end{aligned}$$

~~$$Y = \bar{Q}_B Q_A + \bar{n}$$~~

$$Y = (Q_A + Q_B)n$$

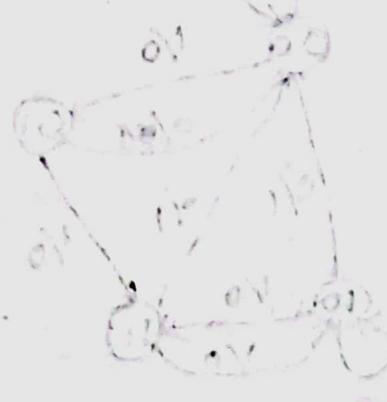


for diagram by equation ~~Q_A+1 , Q_B+1~~

FF \rightarrow equation (2) \oplus (3) or (2) \oplus (3)

state table

present state	input	next state	output		
Q_A	Q_B	n	Q_A+1	Q_B+1	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State diagram

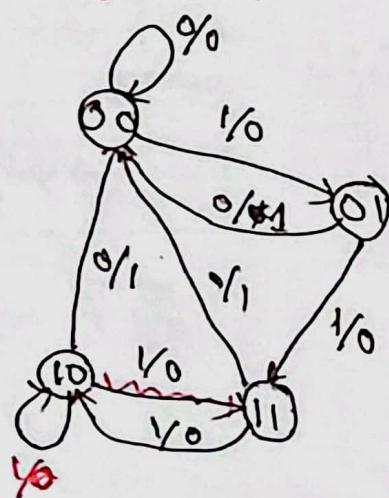

$$J_A = B \quad k_A = B\bar{n}$$

$$J_B = n' \quad k_B = A \oplus n$$

state equation

state table

present state	input	next state	FF	
$q_A \ q_B$	n	$q_{A+1} \ q_{B+1}$	$J_A \ \bar{k}_A$	$J_B \ k_B$
0 0	0	0 1	0 0	1 0
0 0	1	0 0	0 0	0 1
0 1	0	1 1	1 1	1 0
0 1	1	1 0	1 0	0 1
1 0	0	1 1	0 0	1 1
1 0	1	1 0	0 0	0 0
1 1	0	0 0	1 1	1 1
1 1	1	1 1	1 0	0 0

$$J_A \ \bar{k}_A = q_{n+1}$$

0 0 memory


0 1

1 0

1 1

Toggle

state diagram

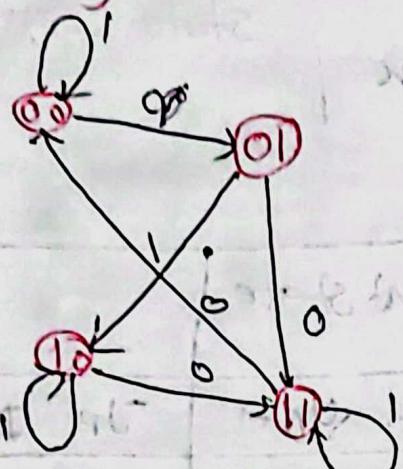

$$T_B = n \cdot T_A + n^2$$

$$N \cdot T_A = g \cdot n \quad n = g \cdot t$$

After solving

	slide	turn	turn	slide	turn	turn	slide	turn
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0
2	0	0	1	0	1	0	0	0
3	0	0	1	0	0	1	0	0
4	0	0	1	0	0	0	1	0
5	0	0	1	0	0	0	0	1

state equation

$$T_A = B_n$$

$$T_B = n$$

$$Y = AB$$


$T \quad S_n = S_{n+1}$
 $0 \quad 0 = \text{memory}$
 $0 \quad 1 = "$

$\backslash \quad 0 = \text{Togge}$
 $1 \quad 0 = "$

state table

present state	input	next state	FF	output
$S_A \quad S_B$	u	$S_{A+1} \quad S_{B+1}$	T_B	T_B
00	0	00	0	0
00	1	01	0	0
01	0	01	0	0
01	1	10	0	1
10	0	10	0	0
10	1	11	0	0
11	0	11	0	1
11	1	00	0	1

state diagram

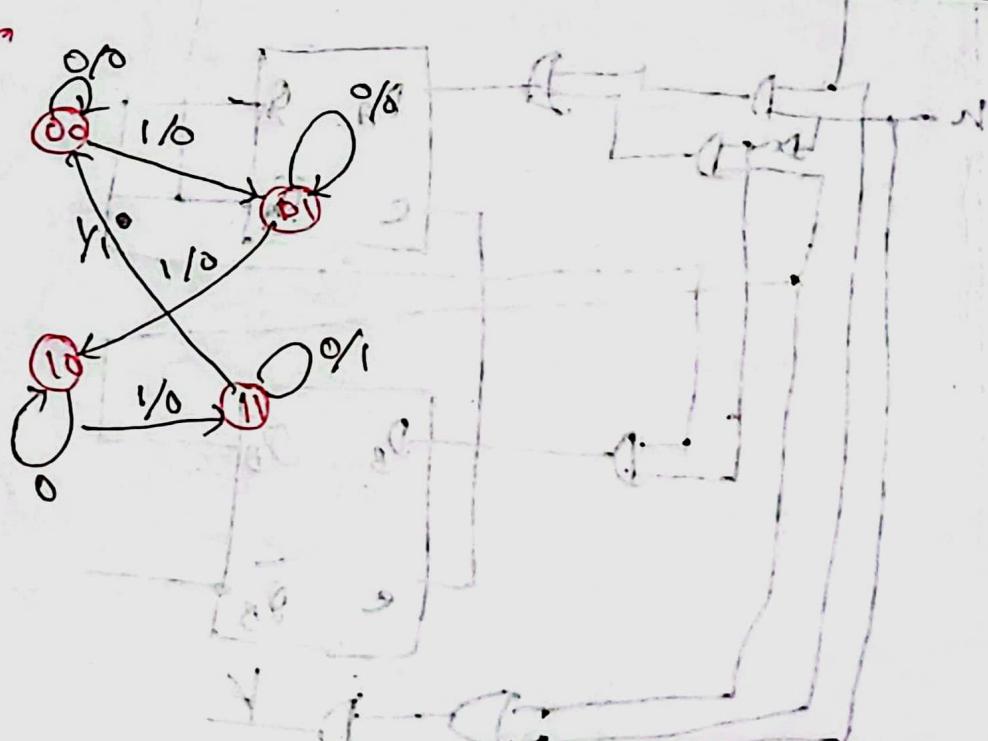

problem

A sequential circuit with two D flip-flops

A and B, one input x , and one output y


y is specified by the following input equation

$$D_A = \bar{A}x + B\bar{x}$$

$$D_B = Ax$$

$$Y = (\bar{A} + B)x$$

Logic diagram

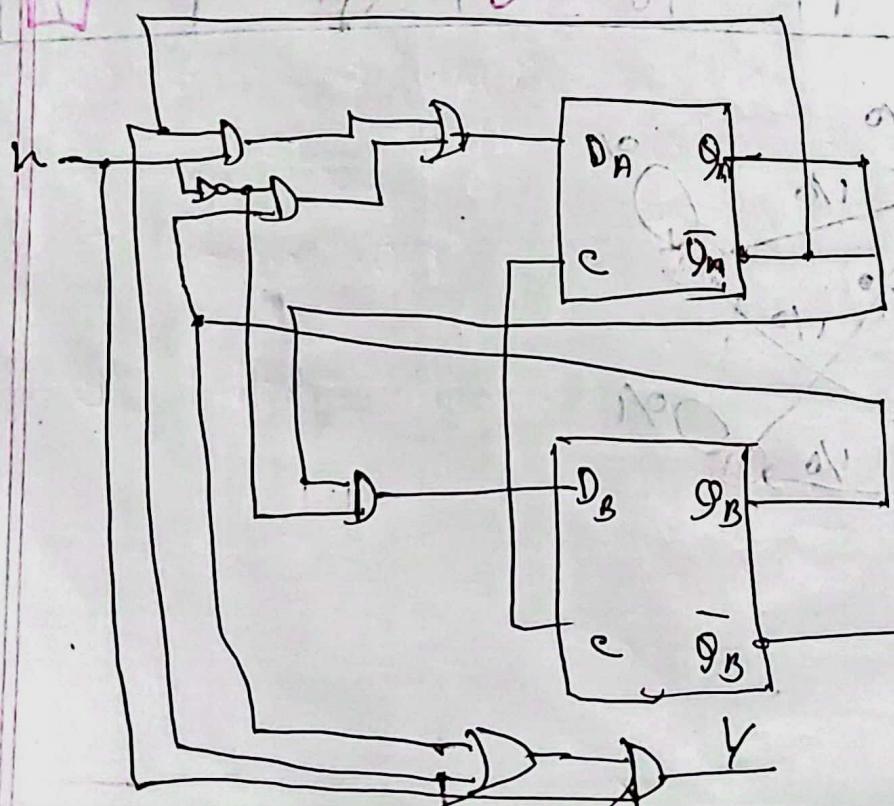


① Logic diagram

② state table

③ state diagram

state table

present state	input	next state	out put	FF
$Q_A \ Q_B$	n	$Q_{A+1} \ Q_{B+1}$	1/1/1/1	$D_A \ D_B$
0 0	0	0 0	0	0 0
0 0	1	1 0	1	1 0
0 1	0	1 0	0	1 0
0 1	1	1 0	1	1 0
1 0	0	0 1	0	0 1
1 0	1	0 0	0	0 0
1 1	0	1 1	0	1 1
1 1	1	0 0	1	0 0

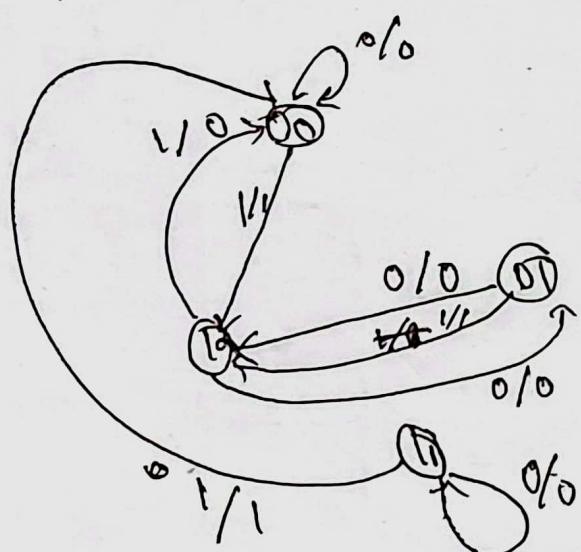

Sequence recognizer

Input (1101)

input 00 **1101101**
output ↓↓↓↓↓↓↓↓

Output द्वितीय अमर्याल्ये आदि previous


input द्वितीय sequence निम्न ता द्वितीय

output (0) आदि आदि निम्न द्वितीय (1)

For solve

- ① state diagram
- ② state table
- ③ equation
- ④ Logic diagram

❖ 0101 Recognize state Diagram

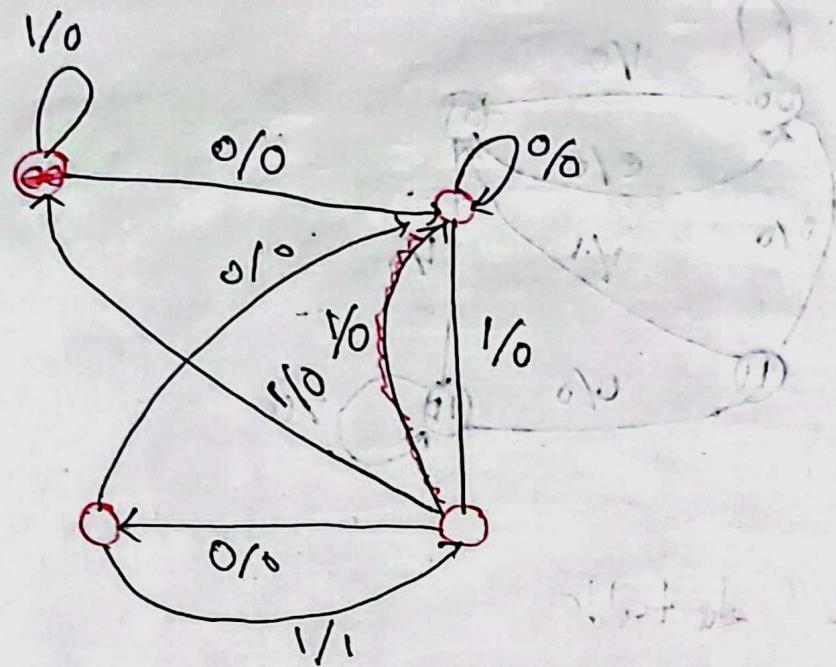


sequence ক্রমান্বয়ীভাবের পরিমাণে ২টি, যদি Recognize
ক্ষয়ায় অবস্থা ৬ টি। Recognize ক্ষয়ের উপরে নথিত
চারটির এর পরিসর step ৬ পরিমাণে।

ନାୟକ ଦୁଇ ହୋରିଲେ ଡାଳେ ଓ Recognize
ଏହି ବାଲୁ ପାଇଁ ରଖିଲା ମାତ୍ର ।

problem
2

(0110) sequence Recognize (JK FF)

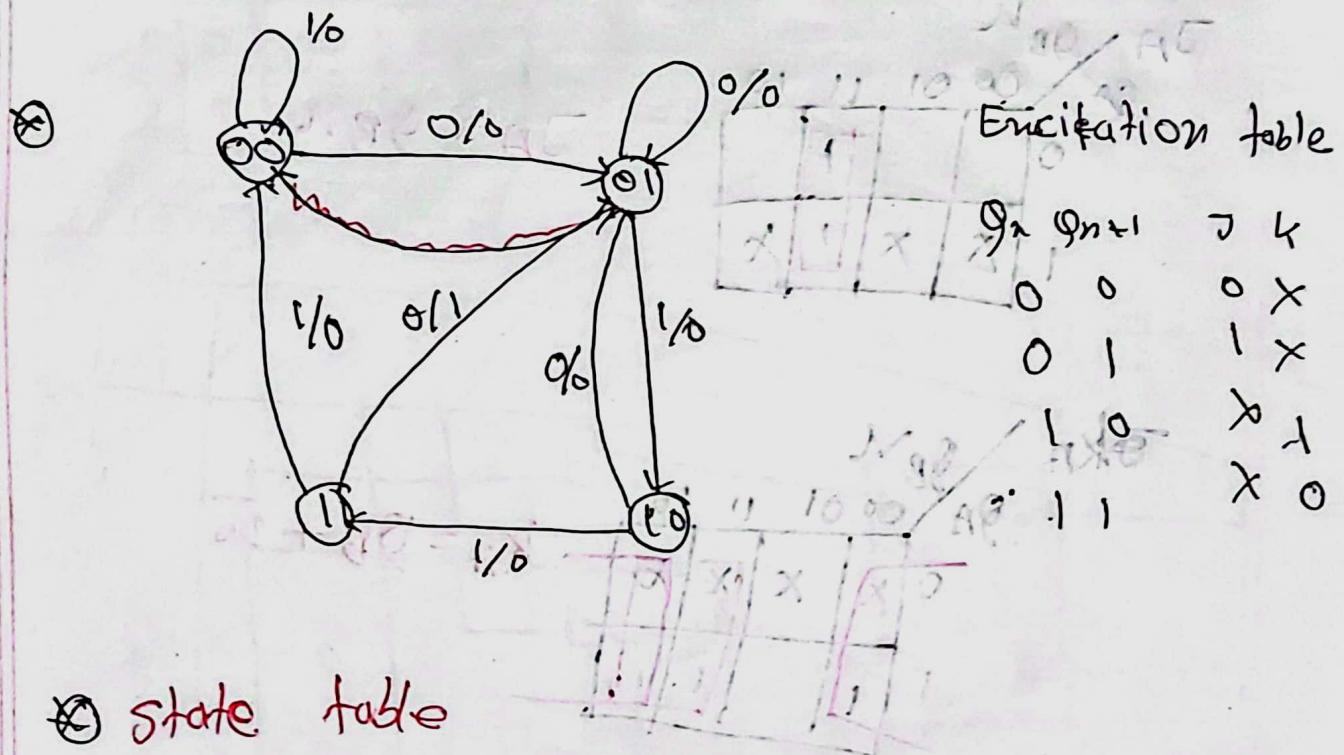

state table

present state	input	next state	output	FF
$q_A \ q_B$	x	$q_{n+1} \ q_{B+1}$	y	$J_A \ k_n \ J_B \ k_B$
0 0	0	0 0	0	0 X
0 0	1	0 0	0	0 X
0 1	0	0 0	0	0 X
0 1	1	1 0	0	1 X
1 0	0	0 0	0	X 1
1 0	1	1 1	0	X 0
1 1	0	0 1	1	X 1
1 1	1	0 0	0	X 0

K-map

$$J_A = \bar{Q}_B \bar{n}$$

		00	01	11	10	
		0	1	1	1	
		1	X	X	1	X
0	0	0	0	1	1	
1	0	1	0	1	1	

$$J_A = \bar{Q}_B \bar{n}$$

$$\bar{Q}_A \bar{Q}_B \bar{n}$$

		00	01	11	10
		0	X	X	X
		1	1	1	1
0	0	0	0	1	1
1	0	1	0	1	1

$$k_A = \bar{Q}_B + \bar{n}$$

$$\bar{Q}_B \bar{Q}_n$$

		00	01	11	10
		0	1	X	X
		1	0	1	X
0	0	0	0	1	1
1	0	1	0	1	1

$$J_B = \bar{Q}_A + \bar{n}$$

$$k_B \bar{Q}_B \bar{n}$$

		00	01	11	10
		0	X	X	1
		1	X	X	1
0	0	0	0	1	1
1	0	1	0	1	1

$$k_B = \bar{n}$$

$Y = Q_A \bar{Q}_B n$

\bar{n}	00	01	11	10
0	0	0	0	0
1	0	0	0	1

$$Y = Q_A Q_B \bar{n}$$

